



## **GN001 Application Guide**

# **Design with GaN Enhancement mode HEMT**

Updated on JAN-24-2018  
GaN Systems Inc.



- [Basics](#)
- [Gate Drive Design considerations](#)
- [Design examples](#)
- [PCB Layout](#)
- [Switching Testing results](#)

***Latest update JAN-18-2018***


Please visit <http://www.gansystems.com/whitepapers.php> for latest version of this document
  
## GaN Enhancement mode High Electron Mobility Transistor (E-HEMT)

- Lateral 2-dimensional electron gas (2DEG) channel formed on AlGaIn/GaN hetero-epitaxy structure provides very high charge density and mobility
- For enhancement mode operation, a gate is implemented to deplete the 2DEG underneath at 0V or negative bias. A positive gate bias turns on the 2DEG channel
- It works just like MOSFET except better switching performance



$I_{DS}$  vs.  $V_{DS}$  characteristics

 


## Common with Si MOSFET

- True e-mode normally off
- Voltage driven - driver charges/discharges  $C_{ISS}$
- Supply Gate leakage  $I_{GSS}$  only
- Easy slew rate control by  $R_G$
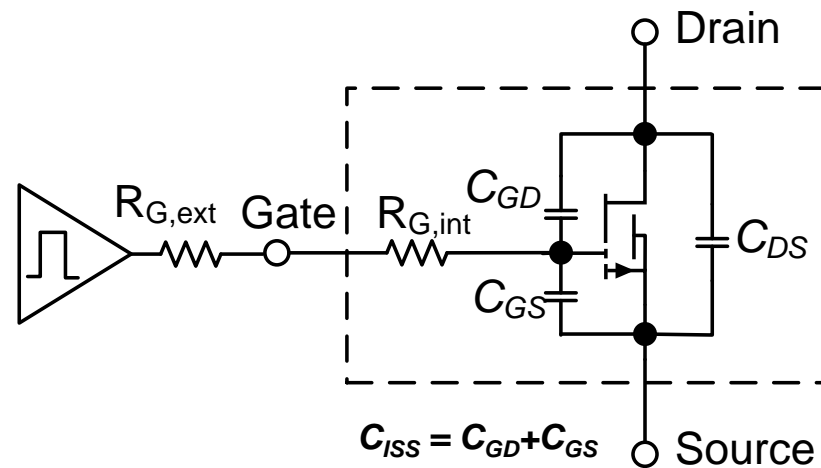
## Differences


- Much Lower  $Q_G$  : Lower drive loss; faster switching
- Higher gain and lower  $V_{GS}$  : +5-6V gate bias to turn on
- Lower  $V_{G(th)}$ : typ. 1.5V



## Versus other e-mode GaN

- More robust gate: +7/-10V DC max rating
- No DC gate holding current required
- No complicated gate diode / PN junction

Gate Bias Level	GaN Systems GaN E-HEMT	Si MOSFET	IGBT	SIC MOSFET
Maximum rating	-10/+7V	+/-20V	+/-20V	-8/+20V
Typical gate bias values	0 or -3/+5-6V	0/+10-12V	0 or -9/+15V	-4/+15-20V

 


	Gate	GaN E-HEMT	MOSFET	Si IGBT
A	ON	$R_{DS(ON)}$		
B	ON	$R_{DS(ON)}$		
C	OFF	$V_{TH} + V_{GS(OFF)}$ $R_{DS(REV)}$		

- No body diode, but 2DEG can conduct in 3rd quadrant – **No need for anti-parallel diode**
- When gate is OFF (during dead time), 2DEG exhibits like a diode with  $V_F = V_{th} + V_{GS(off)}$
- Reduce dead time loss: 1) minimize dead time; 2) Use smaller or avoid negative  $V_{GS}$  if possible

## Reverse Recovery charge $Q_{RR}$ :

- GaN has zero  $Q_{RR}$  making it suitable for **half bridge hard switching** – Replace IGBT
- Si MOSFET can't be used for any half bridge hard-switch circuit due to  $Q_{RR}$
- Excellent reverse recovery of GaN enables new topologies such as bridgeless totem pole PFC


Half bridge turn-on 400V/20A – SJ MOSFET

 

Half bridge turn-on 400V/20A – GaN E-HEMT



- For hard switching:  $t_{d\_pwm}$  must be  $> t_{delay\_skew} + (t_{d(off)} - t_{d(on)})$ :
- Gate turn-on/off delay difference varies with  $R_G$ : typical  $\pm 5ns$  range (GS66508)
- High/low side gate driver delay skew (worst case delay mismatch) usually dominates:
  - Example Silab Si8261 isolated gate driver  $t_{delay\_skew\_max} = 25ns$ . In this case the dead time must be set  $> 30ns$  as minimum
  - However in practical circuit safety margin must be considered: for GS66508 typical **50-100ns** is chosen for dead time
- For soft switching dead time needs to be chosen for achieving ZVS transition
- For 100V: smaller can be used (10-20NS) as 100V driver has better delay matching


 


- [Basics](#)
- [Gate Drive Design considerations](#)
- [Design examples](#)
- [PCB Layout](#)
- [Switching Testing results](#)



GaN switches faster than Si/SiC MOSFETs with  $dv/dt > 100V/ns$

  - GaN shows 4x faster turn-on and  $\sim 2x$  faster off time than state of art SiC MOSFET with similar  $R_{ds(on)}$



Design considerations for driving high speed GaN E-HEMTs:

***Controlling noise coupling from power to gate drive loop should be the first priority:***

- High  $dv/dt$  and  $di/dt$  combined with low  $C_{ISS}$  and  $V_{G(th)}$  → Need to protect gate spikes from going above threshold or maximum rating under miller effect for safe operation
- Gate ringing or sustained oscillation may occur if the design is not done properly and may lead to device failure. We will discuss how to mitigate that in this section
- On the other hand, the switching performance of GaN should not be compromised too much
- This is more critical for 650V hard switching half bridge application as very high  $dv/dt$  could occur at hard turn-on.
- Single end topology has less concern with miller effect, and for resonant ZVS topology the  $dv/dt$  and  $di/dt$  are lower so their design requirement may be relaxed.


***In this section we will walk through the design tips on how to control miller effect and mitigate gate ringing/oscillation, followed by gate driver recommendations***

Gate drive impedance ( $R_G$  and  $L_G$ ) is critical for turn-off, but less at turn-on

*Basic rule: the gate needs to be held down as strong as possible with minimum impedance*


*Miller effect is more prominent at 650V than 100V design due to the higher  $dv/dt$*

## Positive $dv/dt$

 




- Prevent false turn-on
- Strong pull-down (low  $R_G/R_{OL}$ )
- Low  $L_G$  to avoid ringing
- Use negative gate bias, -2 to -3V is recommended

## Negative $dv/dt$

 


- Occurs at turn-on of the complementary switch in half bridge
- Keep  $V_{GS\_pk}$  within -10V
- Strong pull-down (low  $R_G/R_{OL}$ ) and low  $L_G$  for lower ringing
- $V_{GS}$  may bounce back  $>0V$  (LC ringing): ensure  $V_{GS+\_pk} < V_{G(TH)}$  to avoid false turn-on or gate oscillation

- For negative  $dv/dt$ , it is important to have a low-Z path for the reverse miller current to reduce the negative  $V_{GS}$  spike (and the ringing afterwards caused by LC resonance)
  - Pay attention to the  $V_{GS}$  spike around  $V_{DS} < 50V$  due to the change of non-linear  $C_{ISS}/C_{RSS}$  ratio
  - A clamping diode is recommended for gate drive with single output. For gate drive with separate sink output the diode may not be needed depending on the  $R_G$  and  $L_G$  in the circuit
  - For bipolar gate bias, use a TVS diode in series with the clamping diode (or two back to back)
  - $C_{GS}$  may not help in some cases, be careful! ( induce LC resonance with  $L_{gate}$  and  $L_{CS}$ )
  - Negative gate bias can help to prevent false turn-on, but ensure worst case  $V_{gs\_pk}$  within  $-10V$

 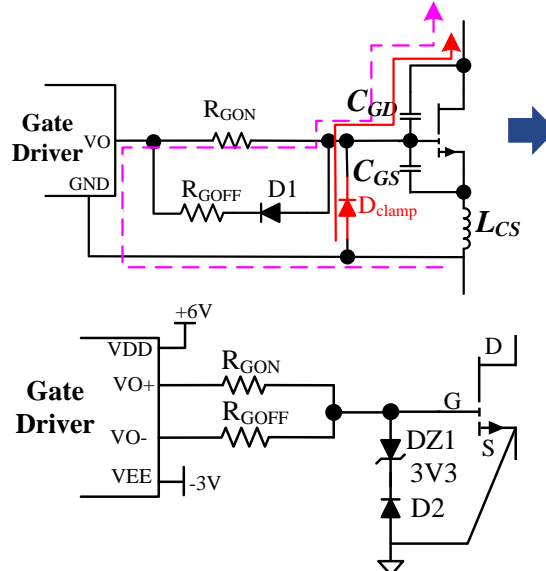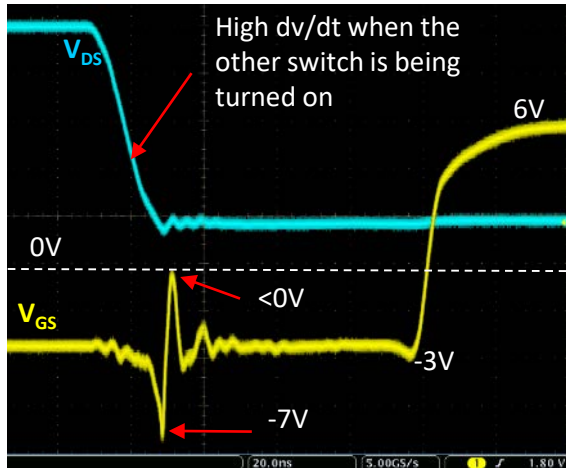

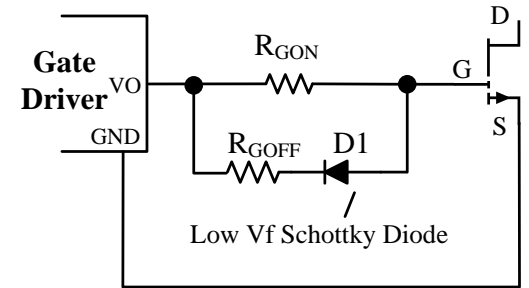
## Select right gate resistor

- GaN E-HEMT speed can be easily controlled by gate resistors
- Critical to choose the right  $R_{G(ON)}/R_{G(OFF)}$  ratio for performance and drive stability
- Separate  $R_G$  for turn-on and off is recommended
- Recommend  $R_{G(ON)}/R_{G(OFF)} \geq \mathbf{5-10}$  ratio for controlling the miller effect
- GaN has extremely low  $Q_g$  and drive loss: most cases 0402/0603 SMD resistors can be used
- Turn on  $R_{G(ON)}$ :
  - Control the turn-on  $dv/dt$  slew rate
  - Too high  $R_{G(ON)}$  slows down switching and increases loss
  - Too small  $R_{G(ON)}$ : High  $dv/dt$  -> Higher switching loss due to the miller turn-on and potential gate oscillation
  - For GS66508: recommend to start with  $R_{G(ON)} = \mathbf{10-20\Omega}$
- Turn off  $R_{G(OFF)}$ :
  - Typical starting value range is  $\mathbf{1-2\Omega}$
  - Provide strong and fast pull-down for robust gate drive



Gate driver w/ single output

 


Gate driver w/ separate outputs

*(Preferred)*


 
## What causes the gate ringing/oscillation?

- Gate over/undershoot and ringing caused by high  $L_G$
- Common Source Inductance  $L_{CS}$  Feedback path from power to gate loop ( $di/dt$ )
- Capacitive coupling via miller capacitor  $C_{GD}$  ( $dv/dt$ )
- Noise coupling via test probe



  
## What to do if gate ringing/oscillation occurs?

- First improve the layout by reducing  $L_G$ ,  $L_{CS}$  and external G-D coupling:
  - Locate driver as close to gate as possible
  - Low inductance wide PCB trace and polygon
  - Use kelvin source connection to minimize  $L_{CS}$
- Select right  $R_G$  to tune turn-on slew rate
- Try negative gate bias (-3V) for turn-off
- At last resort try circuits below to damp the high frequency LC ringing & overshoot:
  - Use a ferrite bead with  $Z=10-20\Omega@100\text{MHz}$  in series with gate. (ferrite bead may increase  $L_G$  but damp the high frequency gate current ringing)
  - RC snubber across G-S: example  $R=3.3/C=200-470\text{pF}$



 
## High side gate drive


- **GaN enables fast switching  $dv/dt > 100kV/us$ :**
  - Minimize Coupling capacitance  $C_{IO}$
  - CM current via  $C_{IO}$  limits CMTI
  - Use isolator/isolated gate driver with high CMTI
- **Full Isolated gate drive:**
  - Best performance
  - Isolation power supply – Minimize inter-winding Capacitance
- **Bootstrap:**
  - Common for lower voltage 100V half bridge design
  - Lower cost and simpler circuit
  - **Choose the bootstrap diode with low  $C_j$  and fast recovery time. Watch for bootstrap diode power loss limit and recovery time for high-frequency operation.**
  - Post-regulation or voltage clamping may be required after bootstrap



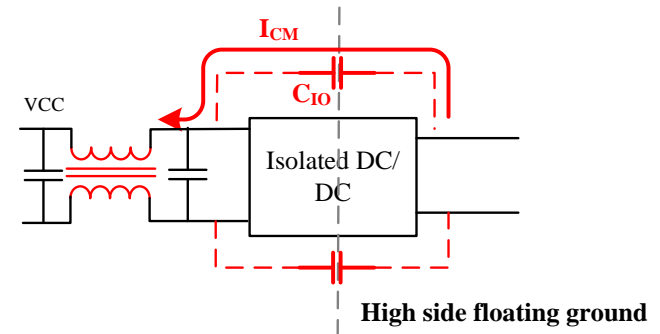Optional common mode choke at input side to suppress CM noise




- Good for low cost 0-6V gate drive
- What is the problem with traditional bootstrap circuit?
  - GaN E-HEMT requires good regulation of gate bias (5-6V bias, max rating 7V)
  - LS free wheeling: Switch node negative voltage overcharges bootstrap capacitors ( $V_{GS} > 7V$ )
  - HS free wheeling: Bootstrap diode voltage drops reduces  $V_{GS}$  below 6V
- Post-regulation or voltage clamping to ensure high side bias is tightly regulated to 6V

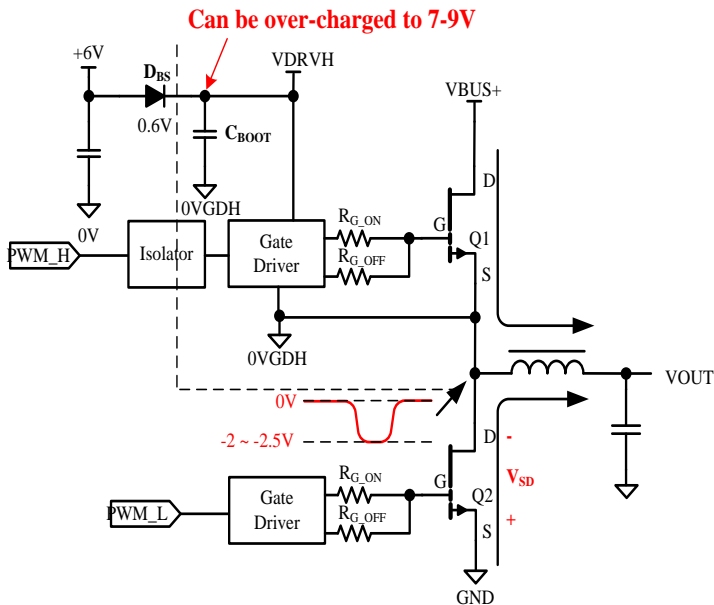


## Bootstrap with post-regulation using +9V for regulated high side bias


Use LDO to regulate to 6V

 

Use Zener diode

 



 
















## Bootstrap for Sync Buck (only need to clamp overcharge, example 100V sync buck)



Simple Zener diode to clamp to 6V



Following drivers have been verified by GS and are recommended for design with our GaN E-HEMTs:

Configurations	Gate Driver/Controller IC	Design resources
<b>650V Half/Full Bridge:</b> 1. DC/DC: LLC, PSFB, Sync Boost/Buck 2. AC/DC: Totem pole PFC, Active Clamp Flyback 3. Inverter, motor drive	 <b>Si8271</b> – Single; <b>Si8273/4/5</b> – HB/Dual -GB (0-6V) or -AB (-3/+6V)	 <a href="#">Si827x Datasheet</a>  <a href="#">Si8271 demo board (GS66508T)</a>  <a href="#">IMS evaluation board User Guide</a>
	 <b>ADuM4121ARIZ</b> (0-6V Drive) <b>ADuM4121BRIZ</b> (-3/+6V Drive)	 <a href="#">ADuM4121 Datasheet</a>
	 <b>ACPL-P346</b> Use -4/+6V gate drive	 <a href="#">ACPL-P346 Datasheet</a>  <a href="#">ACPL-P346 Evaluation Board with GS66508T</a>
<b>80-100V Half/Full bridge</b> 1. 48V DC/DC 2. 48V POL 3. Sync. Buck/Boost 4. Class D Audio 5. Wireless Power Transfer	 <b>LM5113(NRND)</b> : 100V, max 5MHz <b>LMG1205</b> : 80V/5A HB Driver	 <a href="#">LM5113 Datasheet</a>  <a href="#">LMG1205 Datasheet</a>
	 <b>PE29101</b> : 100V, 48V DC/DC, 33MHz <b>PE29102</b> : 60V, Class D Audio, WPT, 40MHz	 <a href="#">PE29100 Datasheet</a>  <a href="#">PE20102 Datasheet</a>  <a href="#">PE29102 Demo board (GS61004B)</a>
	 UPI Semi GaN FET drivers: <b>uP1966A</b> : Dual-Channel GaN driver	 <a href="#">uP1966A GaN Driver</a>  <a href="#">Ultra High Speed 80V HB Driver for GaN Application</a>

Configurations	Gate Driver/Controller IC	Design resources
<b>Low side non-isolated driver for 650V/100V GaN*:</b> 1. Flyback, Push-pull 2. Forward 3. Boost PFC 4. Secondary SR 5. Class E P/A	<b>LM5114/UCC27511:</b> Single Channel, 4A, 5-6V drive <b>UCC27611:</b> w/ internal LDO (5V)	<a href="#">LM5114 Datasheet</a> <a href="#">UCC2751x Datasheet</a>
	<b>uP1964:</b> Internal LDO for 6V drive	<a href="#">uP1964 Datasheet</a>
	Other GaN compatible drivers <b>IXD609SI:</b> Single, 6V drive, high drive current (9A) <b>FAN3122/TC4422:</b> Single, 6V drive, high drive current (9A) <b>FAN3223/4/5:</b> Dual 4A, 6V drive, for push-pull or SR application	
<b>Sync Buck DC/DC (100V GaN):</b> 1. 48V-12V DC/DC	<b>LTC7800:</b> 60V, Sync. Step-Down Controller (up to 2.2MHz, w/ integrated GaN compatible drivers)	<a href="#">LTC7800 Datasheet</a>
<b>Secondary side Rectification (100V GaN):</b> 1. High frequency LLC 2. Flyback	<b>NCP4305A:</b> 5V gate drive clamp, 1MHz max	<a href="#">NCP4305 Datasheet</a>
	<b>SRK2001:</b> Adaptive SR controller for LLC, 5-6V drive for GaN, 500KHz max	<a href="#">SRK2001 Datasheet</a>

[\*] – low side non-isolated drivers can also be used on high side / half bridge configurations by combining with level-shift / signal isolators, see [page 29](#) for design example.

- ❑ [Basics](#)
- ❑ [Gate Drive Design considerations](#)
- ❑ [Design examples](#)
- ❑ [PCB Layout](#)
- ❑ [Switching Testing results](#)

# 650V Isolated Driver Design #1 – 0-6V drive

VDD: 5/9 or 12V depending on system power rail

Optional CM Choke for better noise immunity against dv/dt

### Choose isolated DC/DC PS1:

- 5/9/12V to 9V, 1W, 3kV isolation
- Low  $C_{IO}$  preferred for dv/dt immunity
- Verified/Recommended P/N:
  - RECOM R1S-xx09/HP
  - Mornsun Fxx09XT-1WR2

### PWM Input:


- 3.3V or 5V logic from controller
- Optional RC filter for noise filtering
- Consider driver w/ deglitcher (-IS1 suffix) for noisy environment

### Enable:

- Direct tie to VDDI if not used
- **Recommend filter cap (100nF) close to EN pin to prevent false triggering**

## Si8271-based isolated driver (0-6V drive)

6V LDO for tight  $V_{DRV}$  regulation

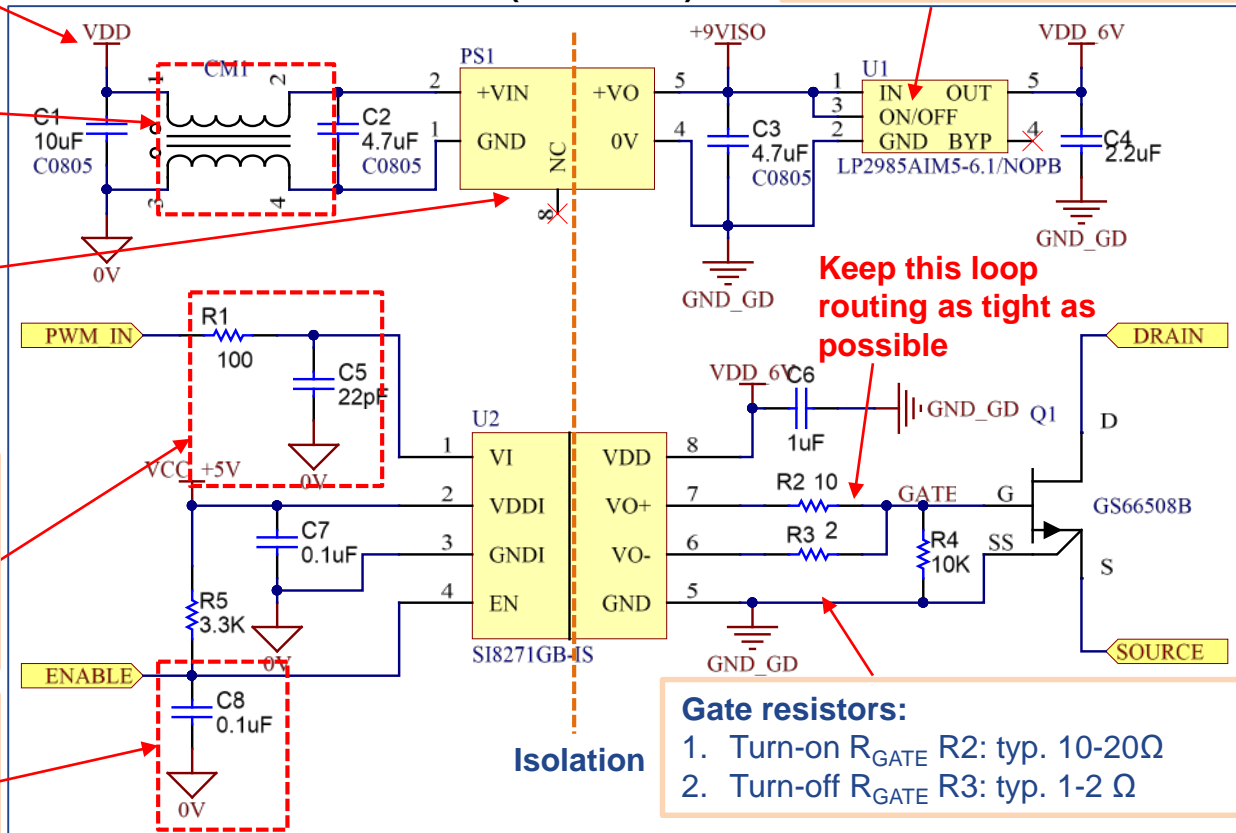


**Keep this loop routing as tight as possible**

**Gate resistors:**  
1. Turn-on  $R_{GATE}$  R2: typ. 10-20 $\Omega$   
2. Turn-off  $R_{GATE}$  R3: typ. 1-2  $\Omega$

**Recommended for high-frequency ZVS application**
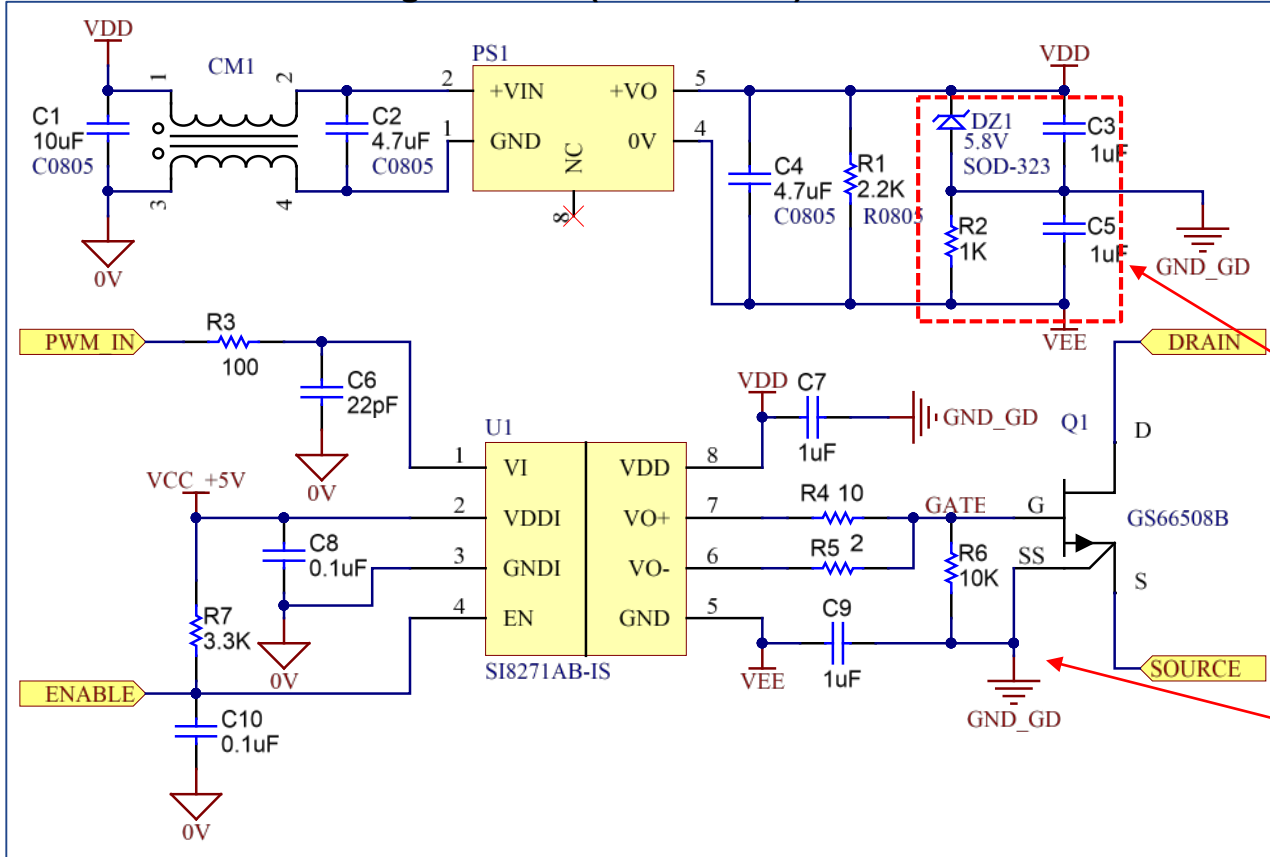
## Si8271-based isolated gate driver (-3/+6V drive)





- Lower risk of cross-conduction and gate oscillation, faster turn-off (lower switching loss)
- Higher reverse conduction loss
- **Recommended for hard-switching or high power applications**

DZ1 and R2 divide 9V into -6V and +3v gate bias. The mid-point is used as a ground 0V which should be connected to the SS of GaN device


- Place bypass cap C7/C8 close to U1 VDD/GND
- Keep loop between U1 and Q1 Gate/SS as tight as possible
- Higher UVLO driver can be used
 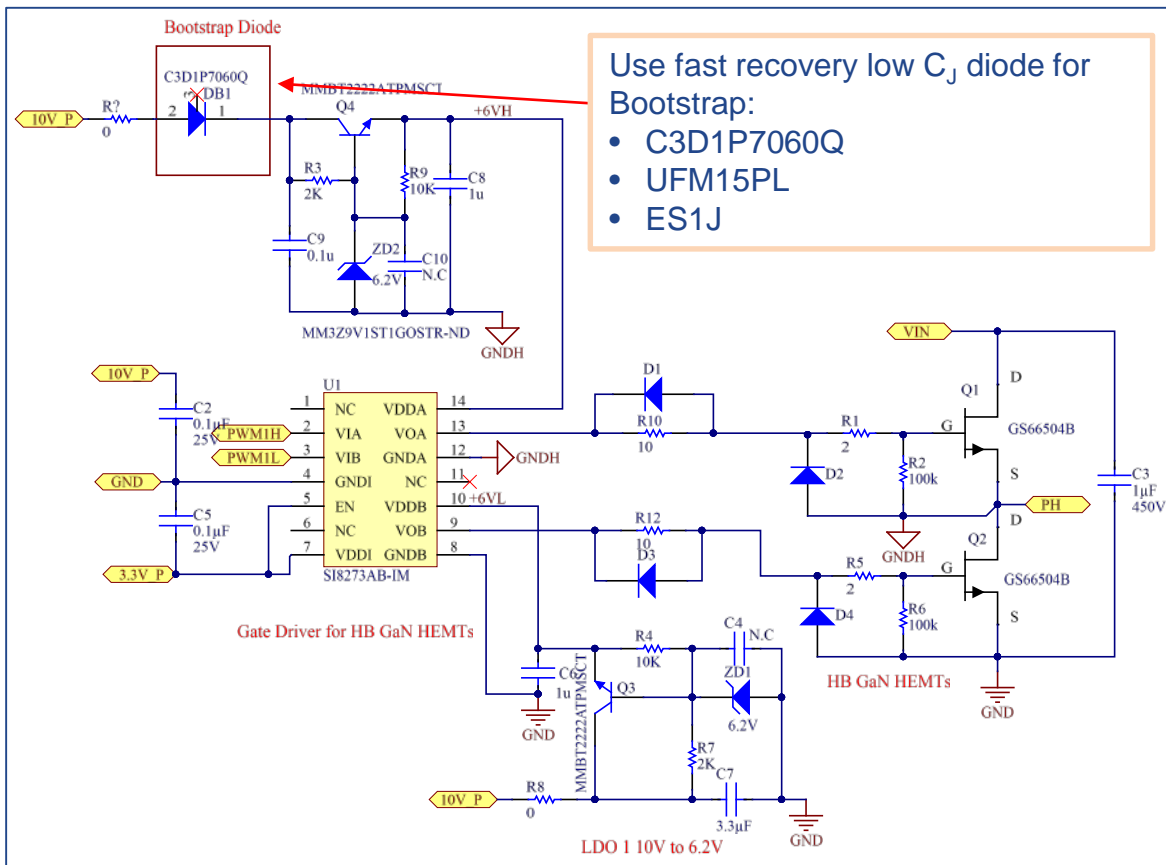
# Bootstrap Half bridge gate driver


Recommended for low cost high frequency soft switch half bridge circuit (ACF, LLC etc)





LLC test waveform (400V/1.3A 600kHz)

 
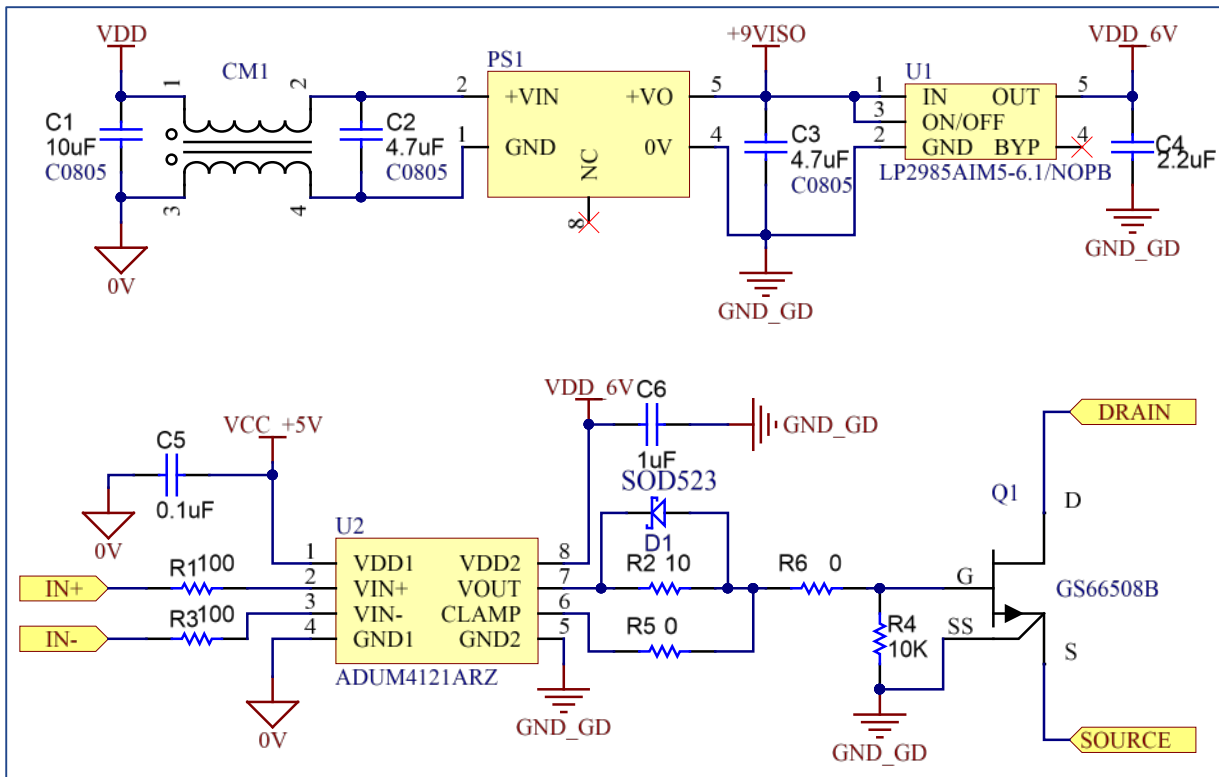
## ADuM4121ARZ-based isolated gate driver for GaN HEMT (0-6V drive)


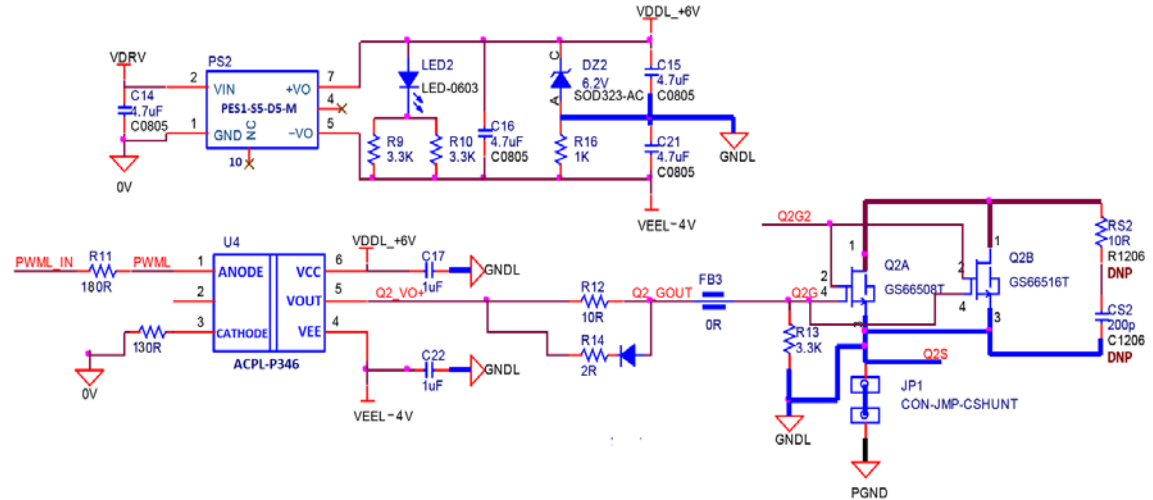 
## Isolated gate driver based on ACPL-P346 (-4/6V)



### Half Bridge Board Reference Design

GaN Systems 650V E-HEMT **GS66508T** (30A/50mΩ) transistor



Broadcom 2.5A gate drive optocoupler, **ACPL-P346**

<https://docs.broadcom.com/docs/ACPL-P346-RefDesign-RM101>


 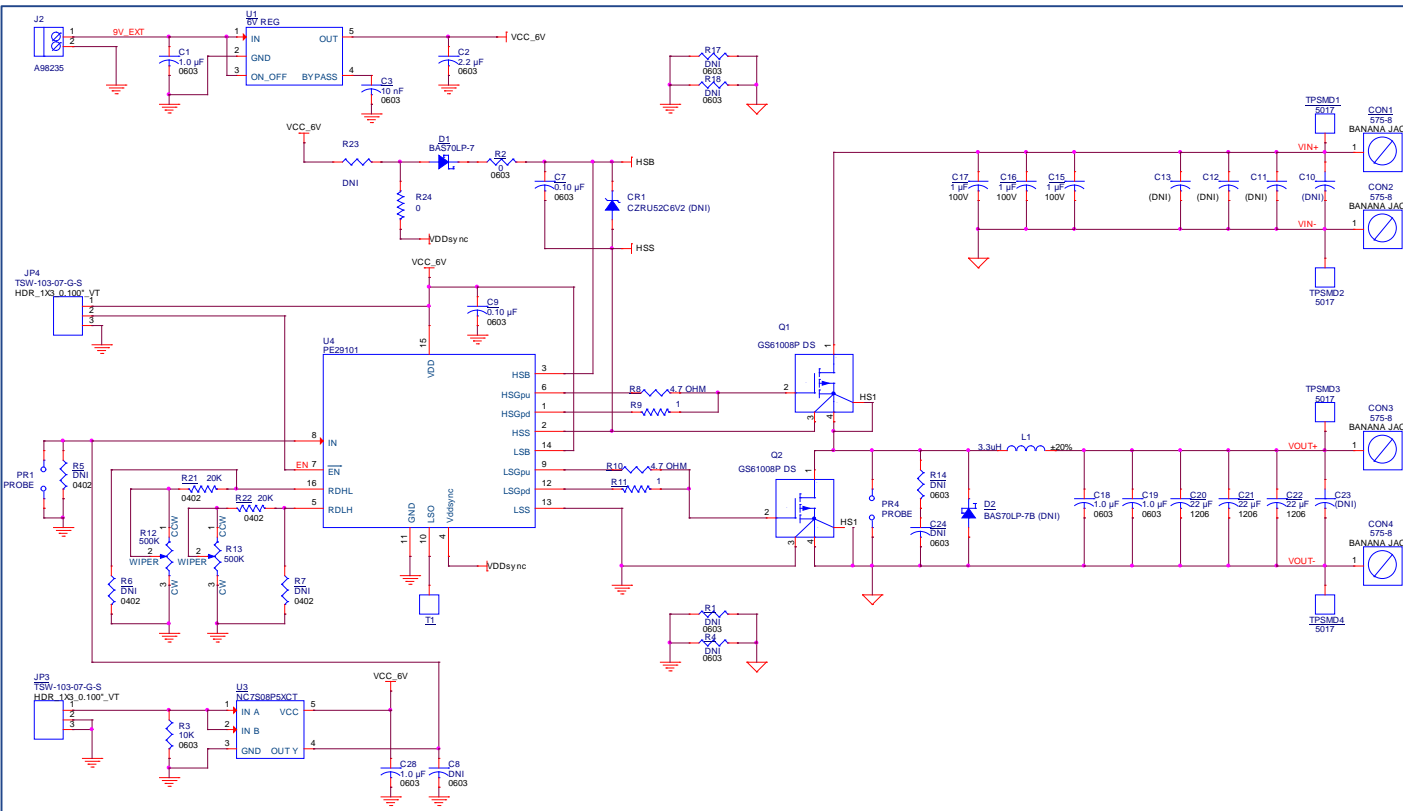
# 100V half bridge GaN driver – PE29101

- 80V HB driver for GaN
- Support 6V gate drive
- 48V DC/DC application
- High frequency (>5MHz)
- Dead time adjustable
- Small low inductance Pkg




<http://www.psemi.com/newsroom/new-products/666336-pe29100-gan-fet-driver>
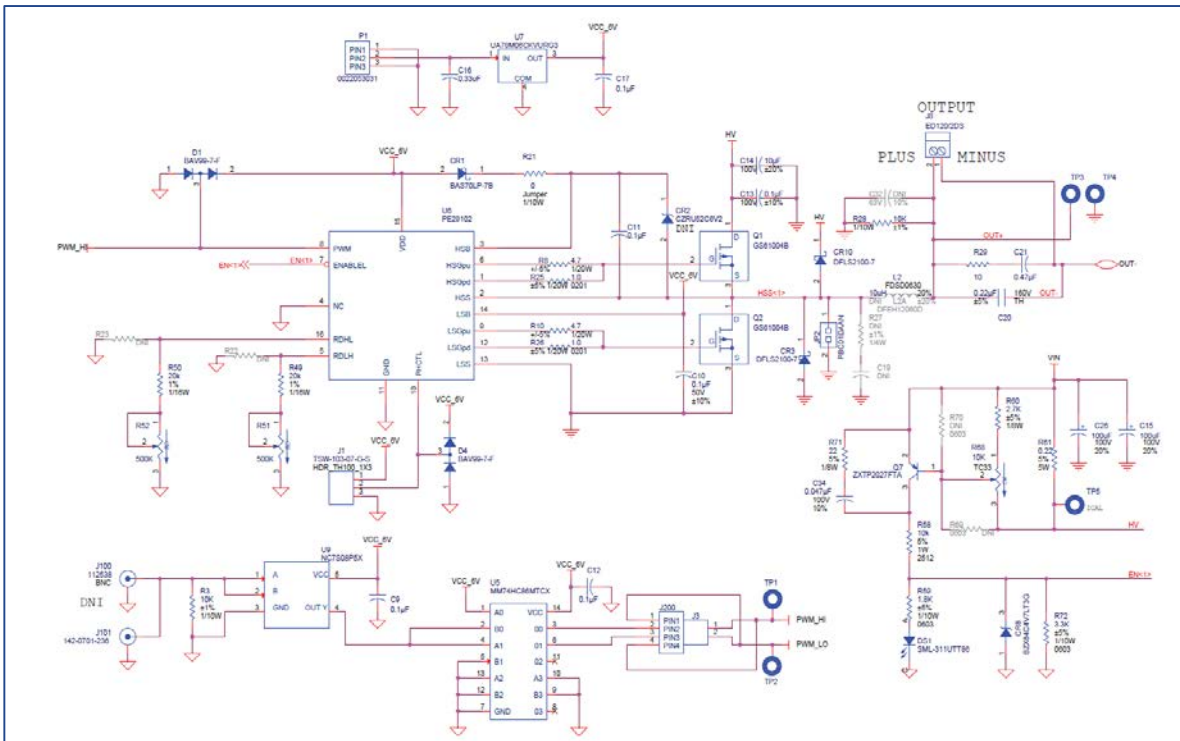
# 100V half bridge GaN driver – PE29102

PE29102 - 60V HB GaN driver optimized for high frequency applications:

- Class D Audio, DC/DC and wireless power charging




100 V GaN Full Bridge EVB optimized for Class D Amplifiers

For more details: <http://www.gansystems.com/gs61004b-evbcd.php>

- For single-ended applications (Class E, Flyback, Push-pull etc), or
- Used to adapt MOSFET gate drive bias to 5-6V drive for GaN (low or high side)



## LM5114 low side driver

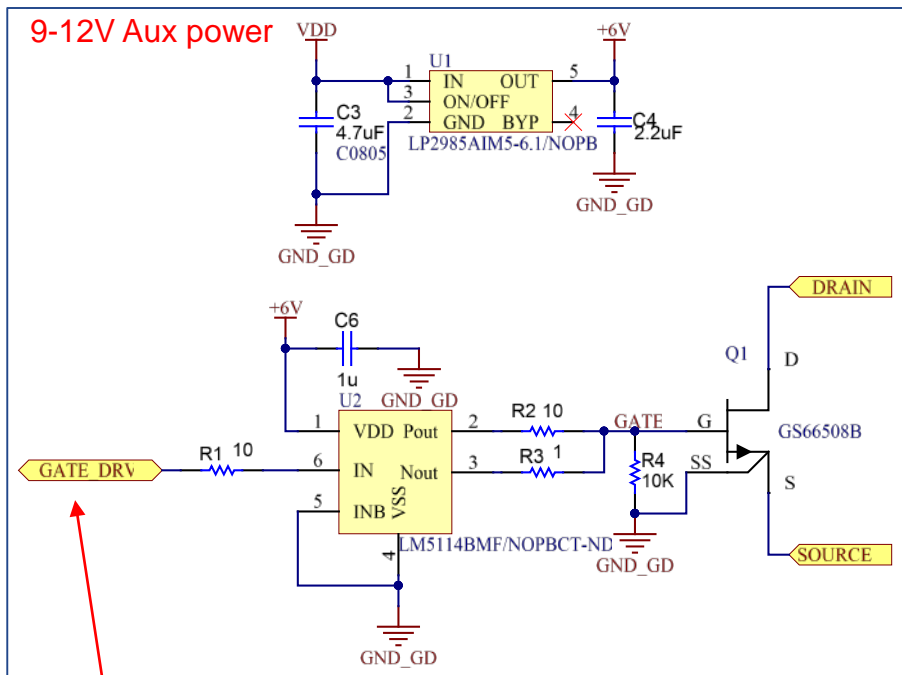

From controller logic signal (3.3/5V) or MOSFET driver output (up to 14V)

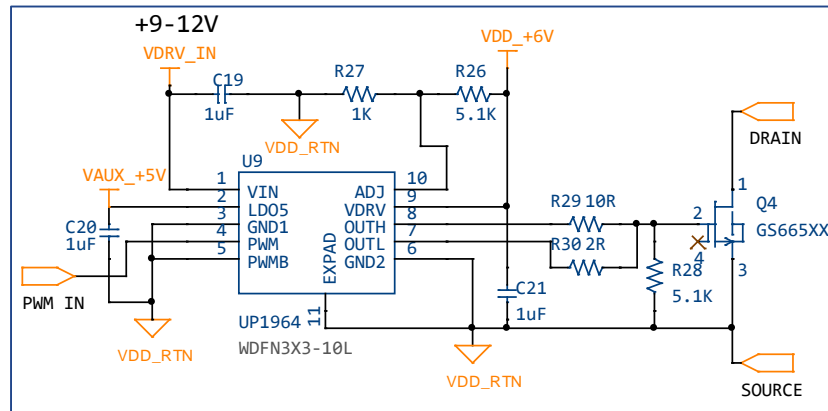 
## uP1964 GaN Driver

- integrated regulator for 6V bias
- 5V LDO
- 




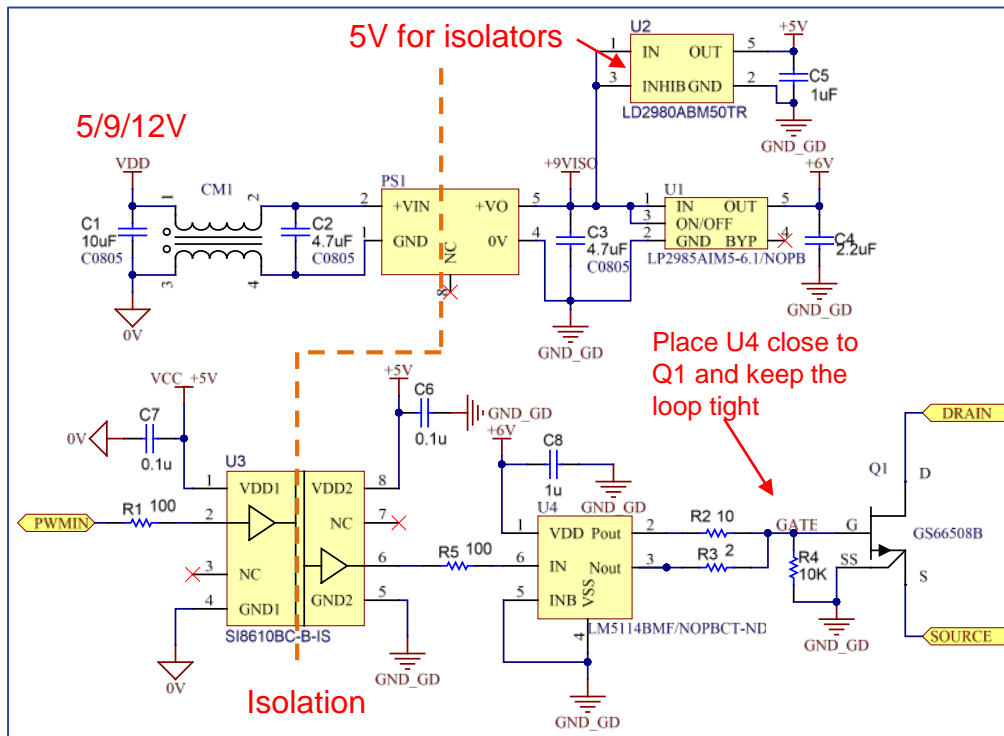
## Isolated GaN driver for high side / half bridge using low side driver + signal isolator or HB driver

- Overcome frequency and drive performance limit of previous isolated driver solution
- Adapt to existing controllers/half bridge driver (ensure the driver is capable of handling high dv/dt)
- Improved gate drive loop by locating LS driver close to GaN



- ❑ [Basics](#)
- ❑ [Gate Drive Design considerations](#)
- ❑ [Design examples](#)
- ❑ [PCB Layout](#)
- ❑ [Switching Testing results](#)

## Traditional PQFN + Wire Bond

  

## Embedded GaNPx™

## Innovative packaging for high speed GaN device:


- Extremely low inductance: high frequency switching
- Near Chip Scale embedded Packaging
- No wire bonding: high reliability
- Better CTE match to PCB: Temp cycle reliability\*
- Lower thermal resistance  $R_{thJC}$



- High  $dv/dt$
- Low  $V_{DS}$  overshoot
- Better EMI

[\*] GaNPx passed 1000hr IPC9701 solder joint reliability test, condition: 12-Layer 2.5mm PCB, 5oz inner copper and 2oz outer copper.




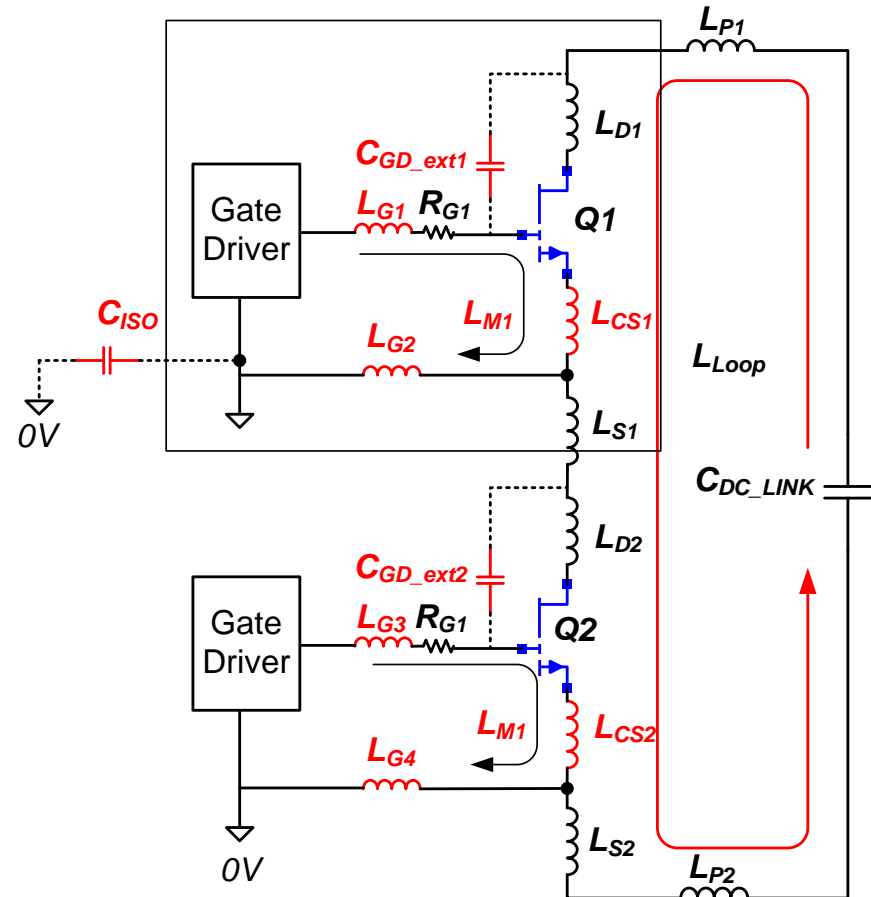
- Design for GaNPx embedded package
  - GaNPx bottom cooled B/P
  - GaNPx Top cooled
  - Thermal design
- Optimize and minimize layout parasitics in following orders :
  1. Common source / mutual inductance  $L_{CS}$
  2. Gate loop inductance  $L_G$
  3. Power Loop inductance  $L_{loop}$
  4. Drain to gate loop capacitance  $C_{GD\_ext}$
  5. Isolation coupling capacitance  $C_{ISO}$



# GaN<sup>Px</sup>™: Bottom cooled B type family

- Embedded package with extremely low inductance
- GS66508B includes dedicated kelvin source pin (SS)
- PCB cooling using thermal pad (S) and vias or metal core PCB for high power application

## GS66508B (650V, 30A, 50mΩ)

  
 
 


Use SS pin for gate return

## GS66504B/GS66502B (650V, 15/7A, 100/200mΩ)



## GS61004B (100V/45A, 15mΩ)

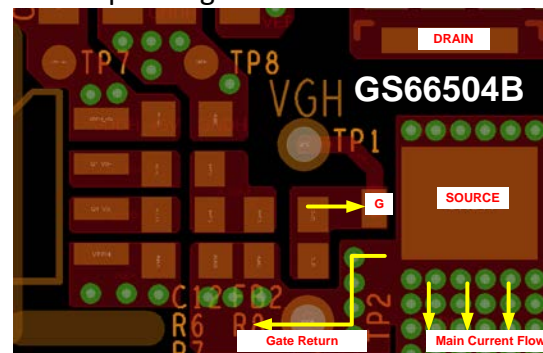  



Create Kelvin source on PCB




# GaN<sub>Px</sub><sup>TM</sup>: Bottom cooled P type

- Similar to B type except substrate (thermal pad) is floating on the package
- Use SS pin for kelvin source connection
- **The thermal pad must be always connected to its source pin on PCB**



GS61008P (100V/90A, 7.5mΩ)

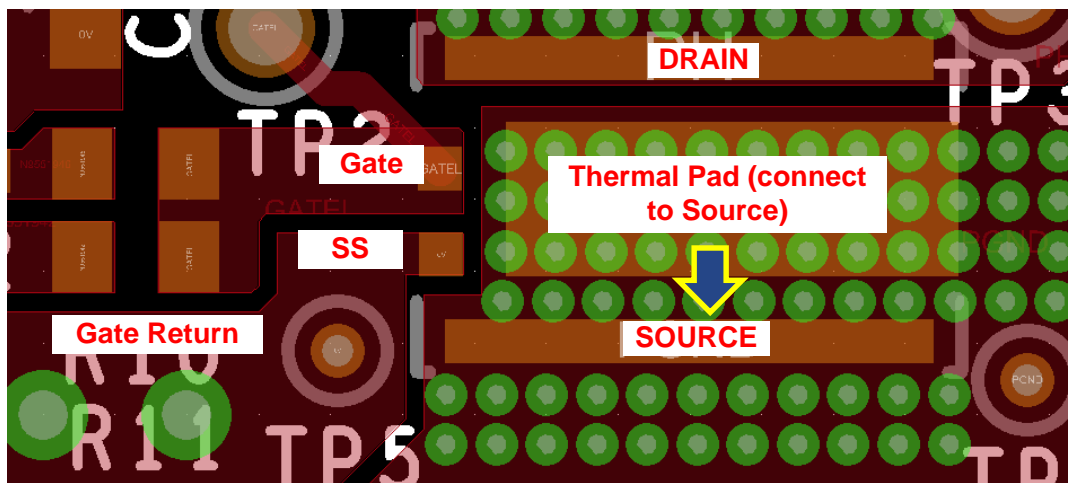 

- 1 Use/create kelvin source to separate drive return and power ground (low  $L_{CS}$ ). Physically separate high current loop and drive loop areas to minimize noise coupling
- 2 Minimize pull-down loop (Gate  $\rightarrow$  R3  $\rightarrow$  U1  $\rightarrow$  C2  $\rightarrow$  GS\_RTN, locate U1 and C2 close)
- 3 Minimize turn-on (pull-up) loop (locate C1 close)
- 4 Isolate and avoid overlap between gate drive and Drain copper pour
- 5 Isolate and avoid overlap from Drain/Source to the control grounds (CMTI,  $dv/dt$ )

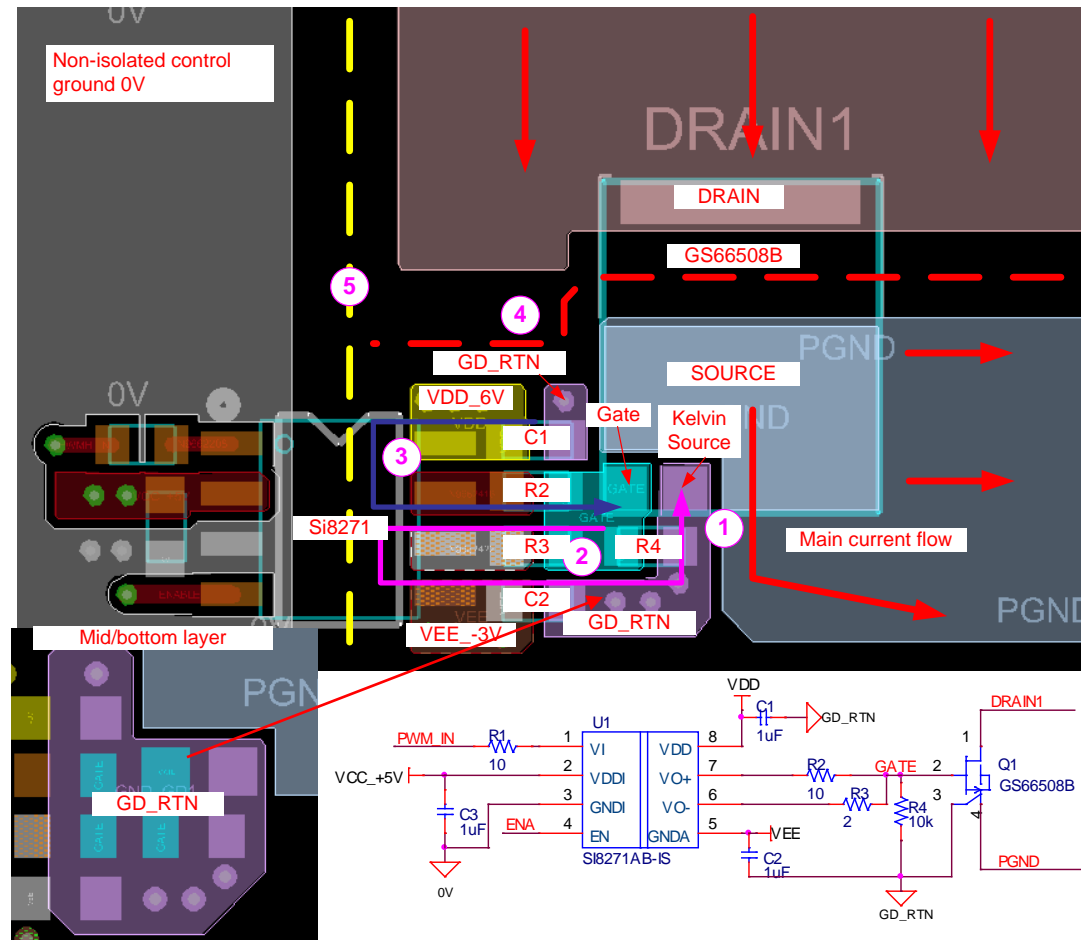

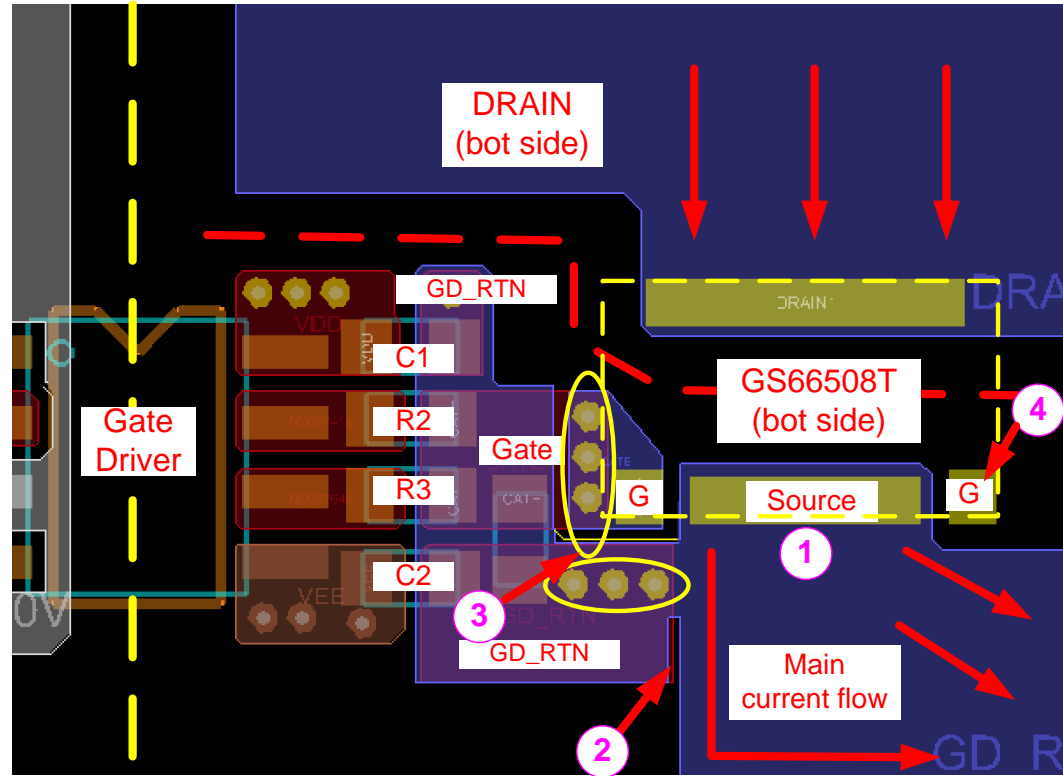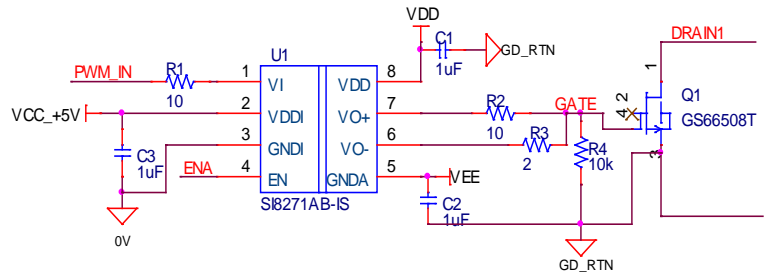- 1 GaNPx T package located at bottom side for heatsink attachment
- 2 Create kelvin connection to the source for Gate drive return (bottom side)
- 3 Use multiple vias for lower gate inductance from bottom to top side
- 4 Use one gate and keep the other floating





Design the half bridge power stage with tight loop and low inductance

## Layout guidance

- Recommend to use 4-Layer PCB
- Use 2<sup>nd</sup> layer as ground return
- Use SMD MLCC decoupling caps and locate them close to GaN
- Use multiple decoupling caps to reduce ESR/ESL and create balanced power loop
- Locate drivers close to the gate
- Use kelvin source for driver return

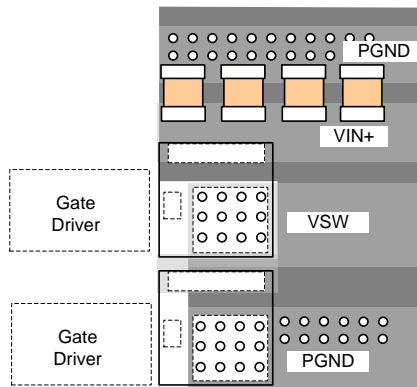
 
### Half bridge design 1

Use layer 2 as ground return (4-layer PCB)




### Half bridge design 2

Only use top layer for power loop

  

 - ❑ [Basics](#)
- ❑ [Gate Drive Design considerations](#)
- ❑ [Design examples](#)
- ❑ [PCB Layout](#)
- ❑ [Switching Testing results](#)



Decoupling Capacitors

Si8271GB Isolated drivers

Recommended Switching node probe position for Eon/Eoff measurement

Isolation Barrier

VGS probe

Optional current shunt  
Use copper foil to short if not used


PWM Signal/+5V VCC connector

VDC-


VDC+

VSW


# GS66508B-EVBDB PCB Layout

 


Top Layer

 

Mid layer 1

 



Mid layer 2

 

Bottom Layer

# Double pulse switching test

- GS66508B hard switched up to 400V/30A

 
 



  
# GS66508 Double pulse switching test

$V_{DS}=400V, I_D=30A$  Hard Switching Turn-on

$V_{DS}=400V, I_D=30A$  Hard Switching Turn-off




- This application guide summarized the key design considerations for GaN Systems GaN E-HEMTs. We started with the fundamental aspects of GaN E-HEMTs and then the gate drive design considerations were discussed. A list of recommended drivers and several gate drive reference designs were provided.
- The second part of this guide focused on the PCB layout and discussed the layout best practice by using GaN Systems Embedded package GaNPx.
- At last a real half bridge evaluation board design following the design recommendations in this document was built and its switching performance was tested.
- The switching test results showed fast and clean hard switching waveforms up to full rated current 400V/30A with minimum ringing/overshoot. This concluded that with optimum gate drive and board layout combined with low GaNPx inductance, GaN E-HEMTs exhibit optimum switching performance

- **Datasheets, spice models:** <http://www.gansystems.com/transistors.php>
- **Evaluation boards:** <http://www.gansystems.com/eval-boards.php>
- **Application notes:** <http://www.gansystems.com/whitepapers.php>
- **PCB Footprint libraries:** [http://gansystems.com/design\\_library\\_files.php](http://gansystems.com/design_library_files.php)
- **FAQ:** <http://www.gansystems.com/faq-e-mode-hemts.php>

Tomorrow's power today™

GaN Systems

 

GaN Systems

[www.gansystems.com](http://www.gansystems.com) • North America • Europe • Asia